## DC Motor Circuit 1

As an electrical schematic a DC motor can be represented as:

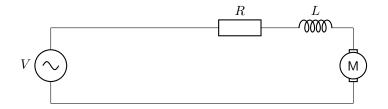


Figure 1: Electrical diagram of DC motor.

By introducing an armature constant of the motor  $K_t$ , the torque the motor produces, T, is related to the armature current of the motor by:

$$T = K_t i \tag{1}$$

Similarly the motor back emf, e, is related to the rotational speed,  $\dot{\theta}$  using the motor constant  $K_e$  by:

$$e = K_e \dot{\theta} \tag{2}$$

From Kirchhoff's law the sum of potential differences in a closed loop must be zero. This leads to:

$$iR + \frac{di}{dt}L = V - k_e \dot{\theta} \tag{3}$$

## 2 Inertia

The inertia of the motor armature must also be considered. From Newton's second law:

$$J\ddot{\theta} + B\dot{\theta} = T \tag{4}$$

Where J is the motor inertial constant, and B the motor damping constant.

## 3 State-space Equations

The following equations:

$$iR + \frac{di}{dt}L = V - k_e\dot{\theta} \tag{5a}$$

$$J\ddot{\theta} + B\dot{\theta} = T \tag{5b}$$

can be written in state-space form. Selecting  $\dot{\theta}$ ,  $\ddot{\theta}$  and i as the state variables:

$$\dot{\theta} = \dot{\theta} \tag{6}$$

For the inertia:

$$J\ddot{\theta} + B\dot{\theta} = T \tag{7a}$$

$$\ddot{\theta} + \frac{B}{J}\dot{\theta} = \frac{T}{J}$$

$$\ddot{\theta} = \frac{T}{J} - \frac{B}{J}\dot{\theta}$$
(7b)

$$\ddot{\theta} = \frac{T}{J} - \frac{B}{J}\dot{\theta} \tag{7c}$$

$$\ddot{\theta} = i\frac{K_t}{J} - \frac{B}{J}\dot{\theta} \tag{7d}$$

(7e)

For Kirchhoff's law:

$$iR + \frac{di}{dt}L = V - k_e \dot{\theta} \tag{8a}$$

$$i\frac{R}{L} + \frac{di}{dt} = \frac{V}{L} - \frac{k_e}{L}\dot{\theta}$$

$$\frac{di}{dt} = \frac{V}{L} - \frac{k_e}{L}\dot{\theta} - i\frac{R}{L}$$
(8b)

$$\frac{di}{dt} = \frac{V}{L} - \frac{k_e}{L}\dot{\theta} - i\frac{R}{L} \tag{8c}$$

(8d)

Using V as the input, and the motor position as the output:

$$\begin{bmatrix} \dot{\theta} \\ \ddot{\theta} \\ \frac{di}{dt} \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & -\frac{B}{J} & \frac{K_t}{J} \\ 0 & -\frac{k_e}{L} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} \theta \\ \dot{\theta} \\ i \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ \frac{1}{L} \end{bmatrix} V$$
 (9a)

$$y = \begin{bmatrix} 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} \theta \\ \dot{\theta} \\ i \end{bmatrix} \tag{9b}$$