

1 DC Motor Circuit

As an electrical schematic a DC motor can be represented as:

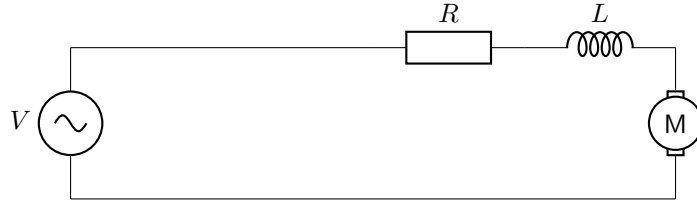


Figure 1: Electrical diagram of DC motor.

By introducing an armature constant of the motor K_t , the torque the motor produces, T , is related to the armature current of the motor by:

$$T = K_t i \quad (1)$$

Similarly the motor back emf, e , is related to the rotational speed, $\dot{\theta}$ using the motor constant K_e by:

$$e = K_e \dot{\theta} \quad (2)$$

From Kirchhoff's law the sum of potential differences in a closed loop must be zero. This leads to:

$$iR + \frac{di}{dt}L = V - k_e \dot{\theta} \quad (3)$$

2 Inertia

The inertia of the motor armature must also be considered. From Newton's second law:

$$J\ddot{\theta} + B\dot{\theta} = T \quad (4)$$

Where J is the motor inertial constant, and B the motor damping constant.

3 State-space Equations

The following equations:

$$iR + \frac{di}{dt}L = V - k_e \dot{\theta} \quad (5a)$$

$$J\ddot{\theta} + B\dot{\theta} = T \quad (5b)$$

can be written in state-space form. Selecting $\dot{\theta}$, $\ddot{\theta}$ and i as the state variables:

$$\dot{\theta} = \dot{\theta} \quad (6)$$

For the inertia:

$$J\ddot{\theta} + B\dot{\theta} = T \quad (7a)$$

$$\ddot{\theta} + \frac{B}{J}\dot{\theta} = \frac{T}{J} \quad (7b)$$

$$\ddot{\theta} = \frac{T}{J} - \frac{B}{J}\dot{\theta} \quad (7c)$$

$$\ddot{\theta} = i\frac{K_t}{J} - \frac{B}{J}\dot{\theta} \quad (7d)$$

$$(7e)$$

For Kirchhoff's law:

$$iR + \frac{di}{dt}L = V - k_e\dot{\theta} \quad (8a)$$

$$i\frac{R}{L} + \frac{di}{dt} = \frac{V}{L} - \frac{k_e}{L}\dot{\theta} \quad (8b)$$

$$\frac{di}{dt} = \frac{V}{L} - \frac{k_e}{L}\dot{\theta} - i\frac{R}{L} \quad (8c)$$

$$(8d)$$

Using V as the input, and the motor position as the output:

$$\begin{bmatrix} \dot{\theta} \\ \ddot{\theta} \\ \frac{di}{dt} \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & -\frac{B}{J} & \frac{K_t}{J} \\ 0 & -\frac{k_e}{L} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} \theta \\ \dot{\theta} \\ i \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ \frac{1}{L} \end{bmatrix} V \quad (9a)$$

$$y = \begin{bmatrix} 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} \theta \\ \dot{\theta} \\ i \end{bmatrix} \quad (9b)$$

4 Current Sensing

As the torque is proportional to the current draw, the torque the motor produces can be found by measuring the current. Current feedback can be achieved by connecting a small resistor from the servo ground to the circuit ground and measuring the voltage drop across it. From Ohm's law $V = IR$ so given the value of the resistor is known priori and V can be measured the current can be found.

This is shown in the diagram below:

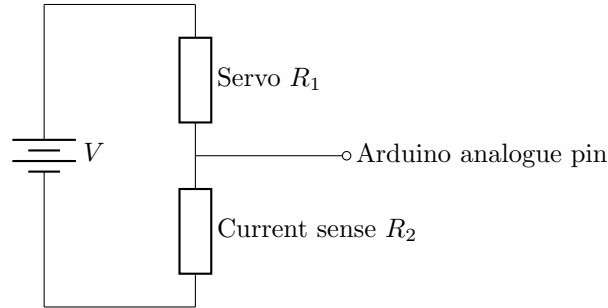


Figure 2: Electrical diagram of current sensing.

The voltage measurement can be done by the Arduino by tapping off of the centre of the potential divider (R_1 and R_2). The current sense resistor R_2 should be small so as to not affect the operation of the servo. A value of 1Ω is sufficient for R_2 .

4.1 Current smoothing

The problem with measuring the current from a servo motor is it is driven by a pulse width modulation (PWM) signal. For a torque controller to work it must receive a continuous value for the current. Smoothing of the current signal can be achieved with a resistor capacitor (RC) circuit:

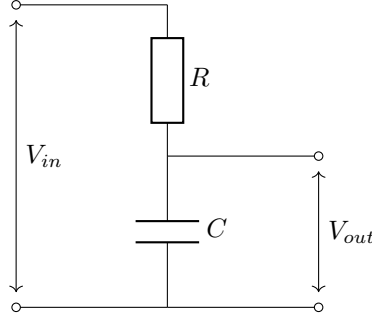


Figure 3: Electrical diagram of RC network.

The current flow is:

$$i(t) = \frac{V_{in}}{R} = \frac{V_R}{R} = C \frac{dV}{dt} \quad (10)$$

Also, for V_{out} :

$$V_{out} = V_C \quad (11a)$$

$$= \frac{Q}{C} \quad (11b)$$

$$= \frac{\int i(t) dt}{C} \quad (11c)$$

$$= \frac{1}{C} \int i(t) dt \quad (11d)$$

$$= \frac{1}{C} \int \frac{V_{in}}{R} dt \quad (11e)$$

$$= \frac{1}{RC} \int V_{in} dt \quad (11f)$$

$$V_{out}(t) = \frac{1}{RC} \int_0^t V_{in} dt \quad (11g)$$

A square pulse wave is a simple case of what the RC network will need to be able to smooth and can be defined as:

$$f(x) = \begin{cases} 1 & \text{if } x < T/2 \\ 0 & \text{if } x > T/2 \end{cases} \quad (12)$$

Therefore for a 5 V input square wave:

$$V_{out}(t) = \frac{1}{RC} \int_0^t V_{in} dt \quad (13a)$$

$$= \frac{1}{RC} \int_0^T \begin{cases} 5 & \text{if } x < T/2 \\ 0 & \text{if } x > T/2 \end{cases} dt \quad (13b)$$

$$= \frac{1}{RC} \left[\int_0^{T/2} 5 dt + \int_{T/2}^T 0 dt \right] \quad (13c)$$

$$= \frac{1}{RC} \left[\int_0^{T/2} 5 dt \right] \quad (13d)$$

$$= \frac{1}{RC} [5t]_0^{T/2} \quad (13e)$$

$$= \frac{1}{RC} \frac{5T}{2} \tag{13f}$$

$$= \frac{5T}{2RC} \tag{13g}$$