

# 1 DC Motor Circuit

As an electrical schematic a DC motor can be represented as:

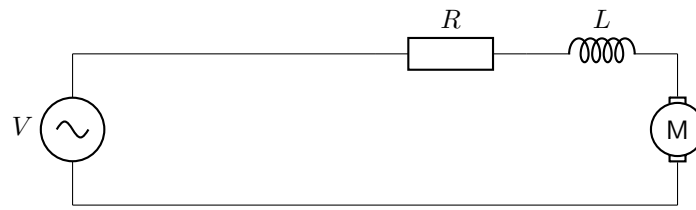


Figure 1: Electrical diagram of DC motor.